

Sub-threshold Circuit Design with Shrinking CMOS Devices

Benton H. Calhoun, Sudhanshu Khanna,
Randy Mann, and Jiajing Wang



Electrical and Computer Engineering
University of Virginia
Charlottesville, VA, USA

Outline

- Sub-threshold Circuits
- Predictive Technology Models
- Obstacles to Sub-threshold Scaling
- Minimizing Energy with Scaling
- Extending Sub-threshold Scaling
- Conclusions

Sub-threshold Operation

  - Sub-threshold logic operates with $V_{DD} < V_T$
- Both *on* and *off* current are sub-threshold “leakage”



Benefits of Sub-threshold

- Sub-threshold benefits: V_{DD} from [1.8,1.0]V to [0.4,0.2]V

Leakage Power Decreases: Power = $V_{DD} I_{off}$

V_{DD} goes down: 2.5X to 9X

DIBL reduces $I_{sub\text{-threshold}}$: 2X to 10X

I_{gate} and I_{GIDL} become negligible

Pleak: 5X to 90X

Energy Consumption Decreases

$$E_{active} = CV_{DD}^2$$

E_{total} /operation minimized in sub- V_T


Reliability Effects Improve

NBTI, EM, TDDB

Main Limitation: Slow Speed, but OK for certain apps

Sub-Threshold Digital Circuits Overview

 - 1972: Sub-threshold theorized for minimum V_{DD} operation (*Swanson & Meindl, JSSC*)
- Major challenges:
 - Reduced Ion/Ioff
 - Variation (local V_T variation, especially)
- Last 5 years: sub-threshold demos of components
 - Logic
 - Memory (SRAM)
 - Micro-processors



Swanson & Meindl, 1972

Primary Use of Sub-threshold Circuits (to date)

- Ultra Low Power (ULP) operation (microsensors, etc.)
- Often long sleep times
- Use an older technology – Is the talk over?

PTM (nm)	$T_{sleep} = 0$	$T_{on} + T_{sleep} = 0.1\text{ms}$	$T_{on} + T_{sleep} = 1\text{ms}$
90	107	107	129
65	77.7	85.5	147
45	58.4	69.8	193
32	47.2	84.0	428
22	41.2	222	1860

Assume 10X less leakage
in standby

Alternative Uses for Sub-threshold

1. Wide range dynamic voltage scaling (UltraDVS)
[Calhoun & Chandrakasan, ISSCC, 2005]
 - e.g. Watchdog sensor, safety critical sensor, etc.
2. Support for high performance
 - e.g. Standby monitor, wakeup circuit, etc.

When to use sub-threshold with scaling:

- Other factors push scaling
- Still need min E for some components *or* times


Outline

- Sub-threshold Circuits
- Predictive Technology Models
- Obstacles to Sub-threshold Scaling
- Minimizing Energy with Scaling
- Extending Sub-threshold Scaling
- Conclusions



Predictive Technology Models

- PTMs from Arizona State (thank you!)
- But, we needed our own version
 - for low power technologies
 - support variation
- Fit to data from industry, papers
- ASU low power PTMs
 - Since became available
 - Fit to ITRS



PTM V_{DD} Scaling

 

PTM MOS Current Scaling

  

PTMs and variation

  



- V_T and L variation
- Select σ based on literature
- Variability impacts functionality (I_{on} vs. I_{off})

Outline

- Sub-threshold Circuits
- Predictive Technology Models
- Obstacles to Sub-threshold Scaling
- Minimizing Energy with Scaling
- Extending Sub-threshold Scaling
- Conclusions

Variation Impacts Noise Margin

 
 
- Noise margin in logic [Kwong '06]
- NAND (poor V_{OL}) to NOR (poor V_{OH}) butterfly



V_{DD} boost and L increase help NM and reduce variability

Variation Impacts Data Retention

  - Noise margin in storage elements
 - Aggravated by smaller devices
 - Sub-threshold bitcells – back-to-back inverters to store





Observations about Obstacles

- V_{DD} floor exists – V_{min} for functionality
 - Logic robustness (noise margin)
 - Data Retention Voltage
- V_{min} may be higher than V_{opt} (for min E)
- V_{min} is a function of L
- Within reason, can trade area for V_{DD} , but increases capacitance...
 - Need to look at min E point for tradeoff

Outline

- Sub-threshold Circuits
- Predictive Technology Models
- Obstacles to Sub-threshold Scaling
- **Minimizing Energy with Scaling**
- Extending Sub-threshold Scaling
- Conclusions


Sub- V_T Minimum Energy Operation

  

Scaling reduces E_{\min} , and raises V_{opt}
 E_{\min} insensitive to small V_{DD} changes

Energy Tradeoff for L

 - From earlier, L increase improves DRV and NM
- Increasing L improves energy at smaller nodes
- L and V_{DD} increase V_{min} , do not cost much energy



Outline

- Sub-threshold Circuits
- Predictive Technology Models
- Obstacles to Sub-threshold Scaling
- Minimizing Energy with Scaling
- Extending Sub-threshold Scaling
- Conclusions


What else to do?

- L and V_{DD} are general knobs, but for sensitive circuits, use context specific response
- Leverage strong knobs (voltages and topology)
- One example: SRAM
 - Alternative bitcells
 - Combine with assist methods

Improve Write Noise Margin

* 8T/10T cell has the same poor write NM as 6T

 - Goal
 - Weaken pull-up FET
 - Strengthen pass-gate FET
- Knobs
 - Size pass-gate to pull-up ratio (not efficient)
 - Collapse Bitcell V_{DD}
 - Boost WL V_{DD}
 - Boost VBP




Bitcell V_{DD} collapse gives adequate writability to 22nm

Use V_{DD} collapse (plus others?) to fix WNM

Improve Read Access

 8T bitcell @ $V_{DD}=0.5V$
256-cell per BL



- To combat large V_T variation, two or more knobs must be used simultaneously
 - boosted footer voltage to improve reading 1
 - boosted WL to improve reading 0

Conclusions

- Scaling sub-threshold makes sense for specific cases, but NOT for ULP only
- Logic NM and DRV (more fundamental) limit voltage scaling in newer technologies
- L and V_{DD} upscaling help
- Customization necessary for sensitive circuits
- Thank you. Any questions?